

Lilo Heinrich

1. V_{in}

2. V_{in}

V_{out}

$R_2 = 10k$

$R_1 = 1k$

2.5V

②

High-Pass ($\omega \gg 1\text{Hz}$) Amplify ($G \approx 10$)


Low-Pass ($\omega \ll 10\text{Hz}$) Amplify ($G \approx 10$)

Output: V_{out}

$$w = \frac{1}{2\pi RC} \rightarrow RC = \frac{1}{2\pi w}$$


Low cutoff freq: 0.5 Hz
High cutoff freq: 5 Hz

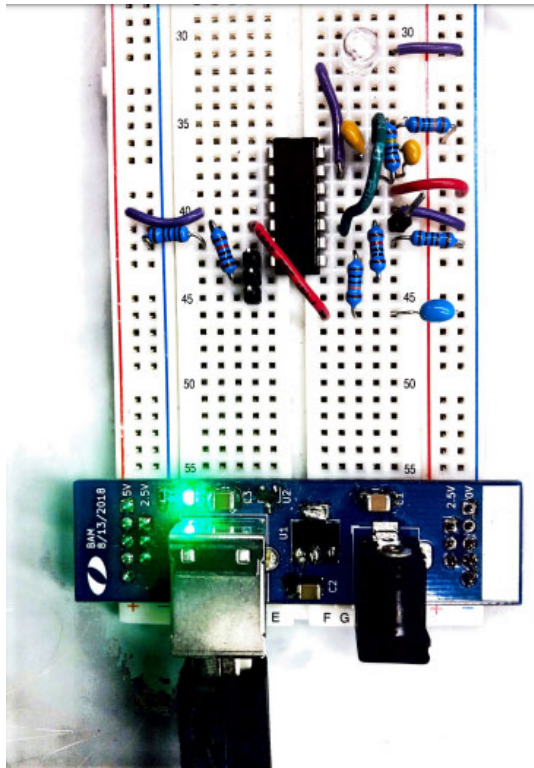Picture of my actual circuit. It has minimal loopy wires but is slightly crowded. Analog discovery disconnected to not obscure the circuit.



Circuit Output

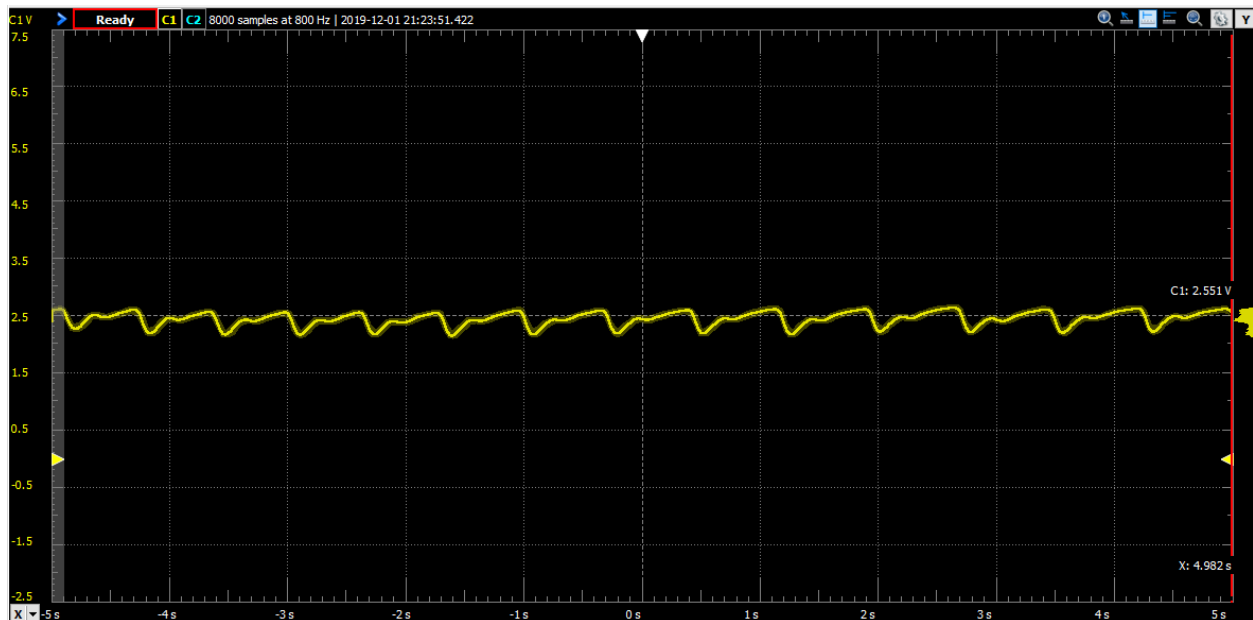Here is a clean trace of my pulse using this circuit:



Obviously, the graph is showing a pulse approximately twice every second, perfectly normal for a heartbeat. This signal looks correct, going by face validity.